

The background of the slide is a composite image. On the left, a white and black robotic arm is shown in profile, reaching out towards the center. The background features a series of DNA double helix structures that recede into the distance, and on the right, a row of server racks. A large, semi-transparent purple circle is centered over the text.

ELEC1100: Introduction to Electro-Robot Design

Lecture 9: Kirchhoff's Laws




FROM LAST LECTURE

- ❖ Circuit analysis: finding I_B and I_C in transistor circuit

$$I_B \approx \frac{V_{in} - 0.7V}{1.08M\Omega}$$

with $V_{in}=5V$
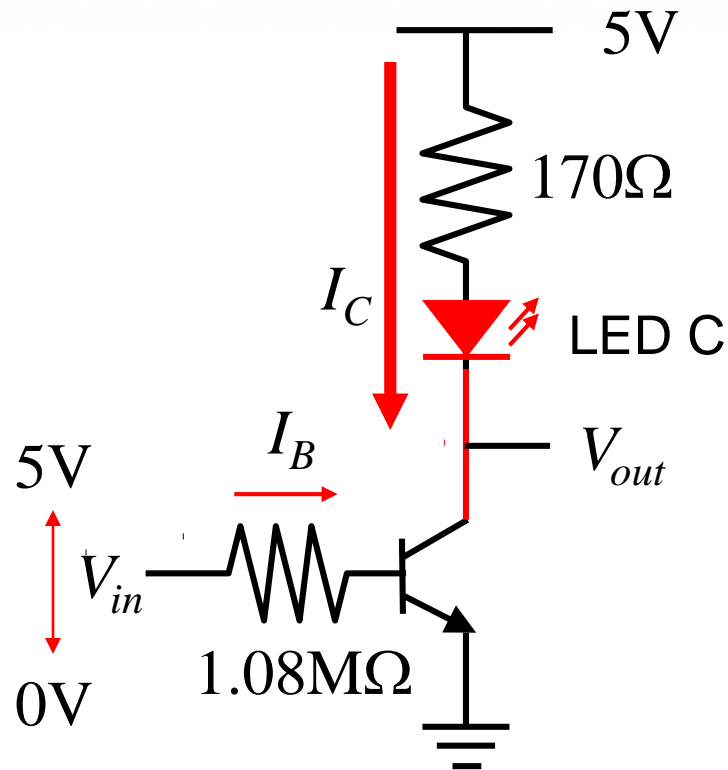
$$I_B \approx \frac{5V - 0.7V}{1.08M\Omega} = 4\mu A$$



$$I_{Cmax} \approx \frac{5V - 0.7V}{170\Omega} = 25mA$$

$$I_C = \beta I_B = 0.4mA$$




COMPLEX RESISTOR NETWORK

- ❖ A general circuit can be very complicated
- ❖ Learn systematic way to analyze circuit like this

Kirchhoff's Current Law

Kirchhoff's Voltage Law

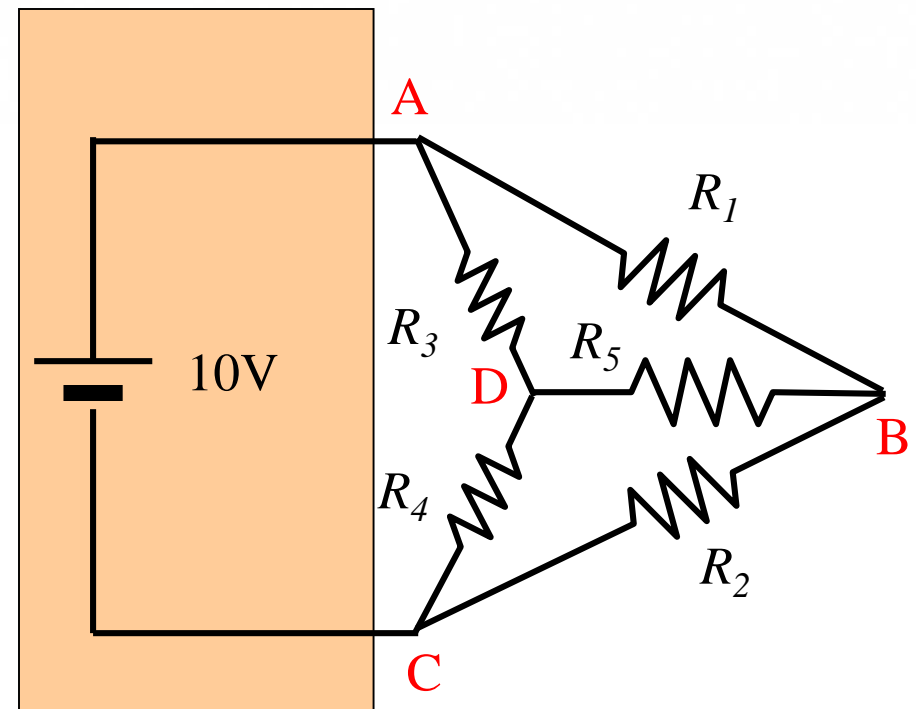


consists of 4 nodes and 6 branches





NODES AND LOOPS

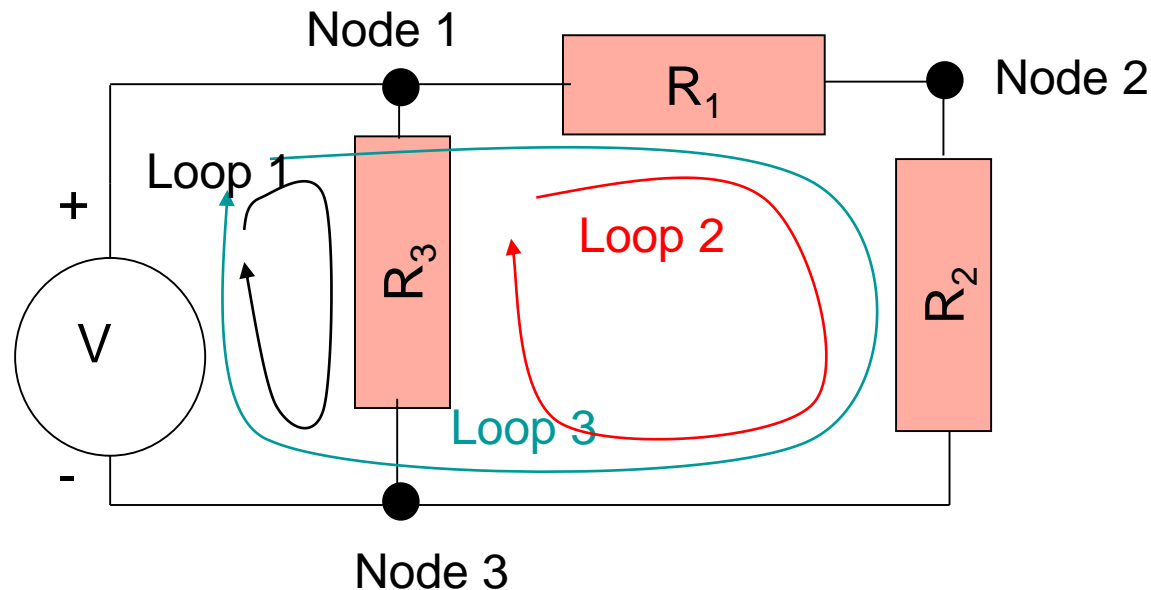- ❖ **Node**: all points connected by a wire, has the same voltage anywhere on the wire
- ❖ **Circuit branch**: circuit element between 2 nodes




- ❖ **Loop**: any circuit branch that ends at the same starting node





CURRENT AND VOLTAGE DIRECTIONS

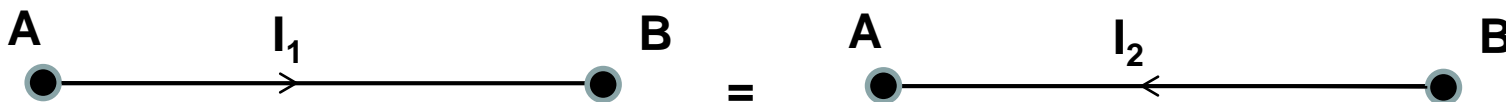- ❖ If current flows in one direction is defined as +ve, flow in the other direction is -ve.



$I_1 = I_{AB}$ = current flow from A to B

$I_2 = I_{BA}$ = current flow from B to A

$$I_1 = -I_2 \quad I_{AB} = -I_{BA}$$


- ❖ Voltage drop also has direction

V_{AB} = voltage drop from Node A to Node B

V_{BA} = voltage drop from Node B to Node A


$$V_{AB} = -V_{BA}$$



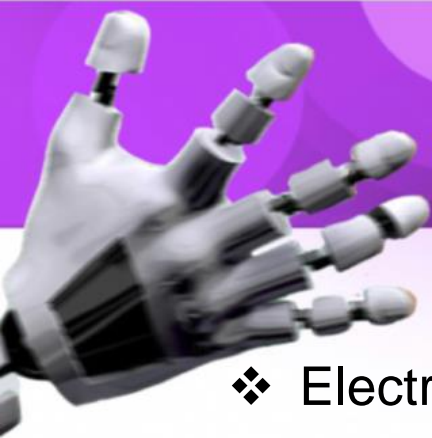

KIRCHHOFF'S CURRENT LAW (KCL)

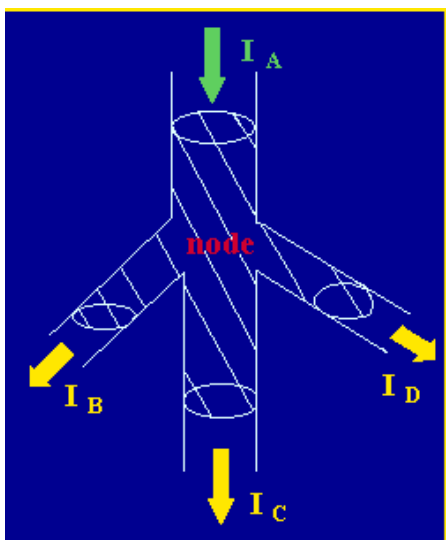- ❖ Electrons can neither be created or destroyed; if it leaves someplace, it has to go to somewhere else
- ❖ The algebraic **sum of all branch currents** entering and leaving a node is zero at all instants of time



➤ By KCL

$$I_A = I_B + I_C + I_D$$


or
$$I_A + (-I_B) + (-I_C) + (-I_D) = 0$$





KIRCHHOFF'S VOLTAGE LAW (KVL) [1]

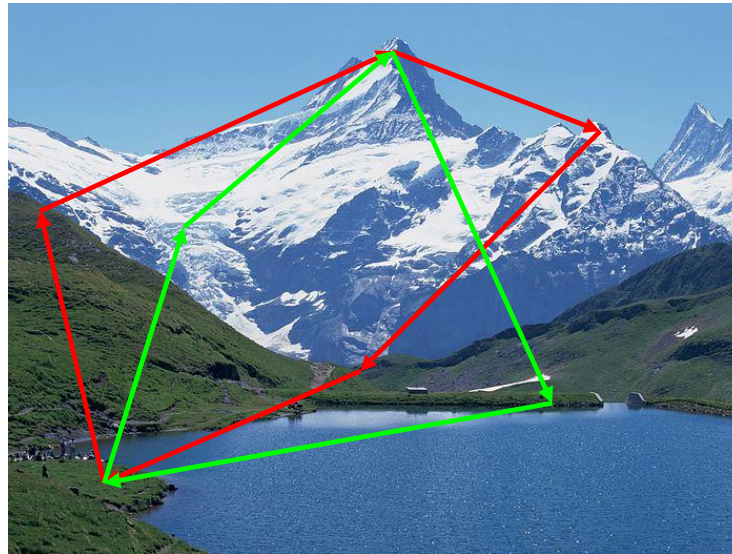- ❖ The algebraic **sum of all branch voltages** around any close loop of a network is zero at all instants of time






KIRCHHOFF'S VOLTAGE LAW (KVL) [2]

- ❖ The algebraic sum of all branch voltages around any close loop of a network is zero at all instants of time

- ❖ Example:

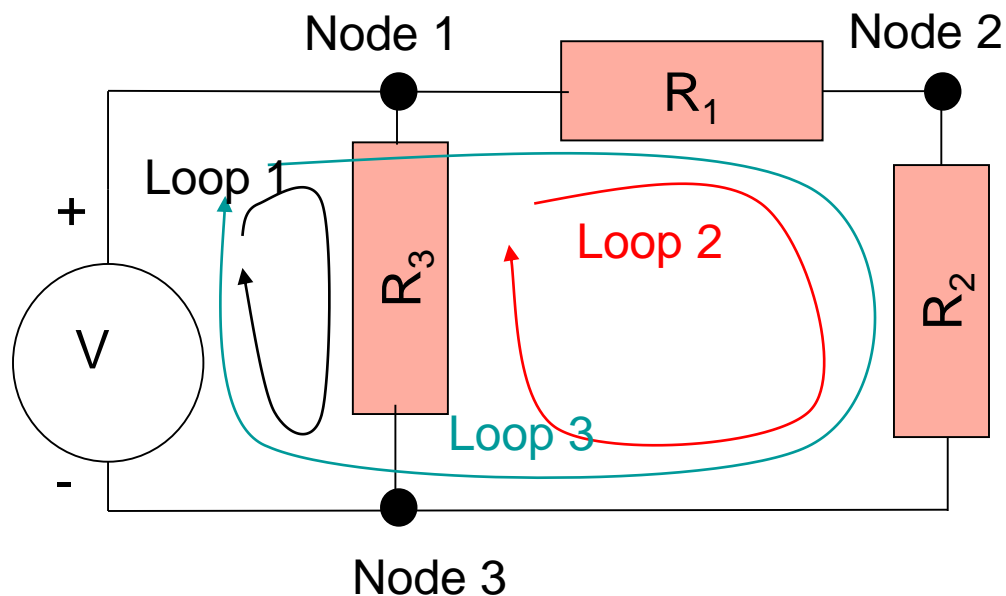

➤ By KVL

L1: $V_{13} - V = 0$

L2: $V_{12} + V_{23} + V_{31} = 0$

L3: $V_{12} + V_{23} - V = 0$





CIRCUIT ANALYSIS

- ❖ Given an electronic circuit network, **circuit analysis** is the process of finding the **voltage** across and the **current** through each component of the network
- ❖ We can use **KCL** and **KVL** to help us to analyze the electronic network systematically






KVL EXAMPLE

❖ Step 1: define the loops

❖ Step 2: write the loop equations

$$\text{L1: } V_{13} - V = 0$$
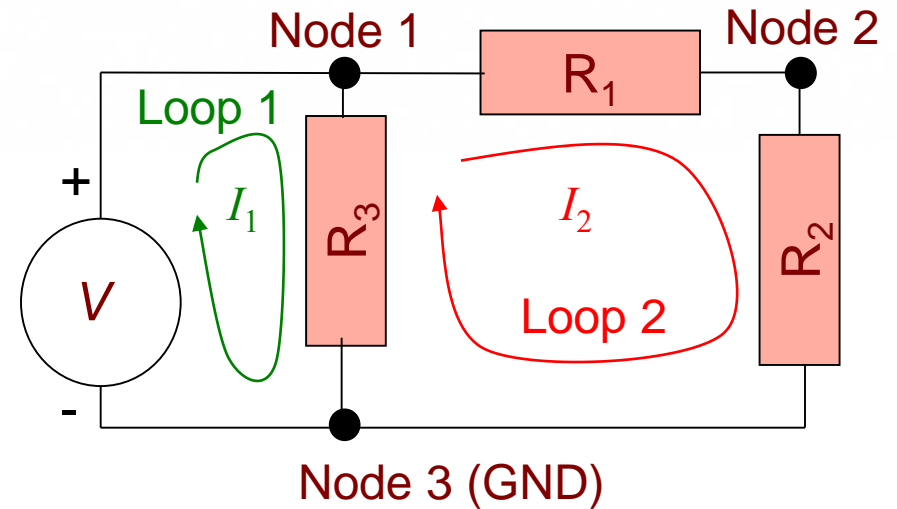
$$\text{L2: } V_{12} + V_{23} + V_{31} = 0$$



❖ Step 3: write all voltages in terms of loop currents

$$\begin{cases} (I_1 - I_2)R_3 - V = 0 \\ I_2R_1 + I_2R_2 + (I_2 - I_1)R_3 = 0 \end{cases} \Rightarrow \begin{cases} R_3I_1 - R_3I_2 = V \\ -R_3I_1 + (R_1 + R_2 + R_3)I_2 = 0 \end{cases}$$

❖ All loop currents (and then node voltages) can be solved




KVL: NUMERICAL EXAMPLE

❖ KVL

$$\begin{cases} R_3 I_1 - R_3 I_2 = V \\ -R_3 I_1 + (R_1 + R_2 + R_3) I_2 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} 25I_1 - 25I_2 = 5 \\ -25I_1 + (75 + 50 + 25)I_2 = 0 \end{cases}$$
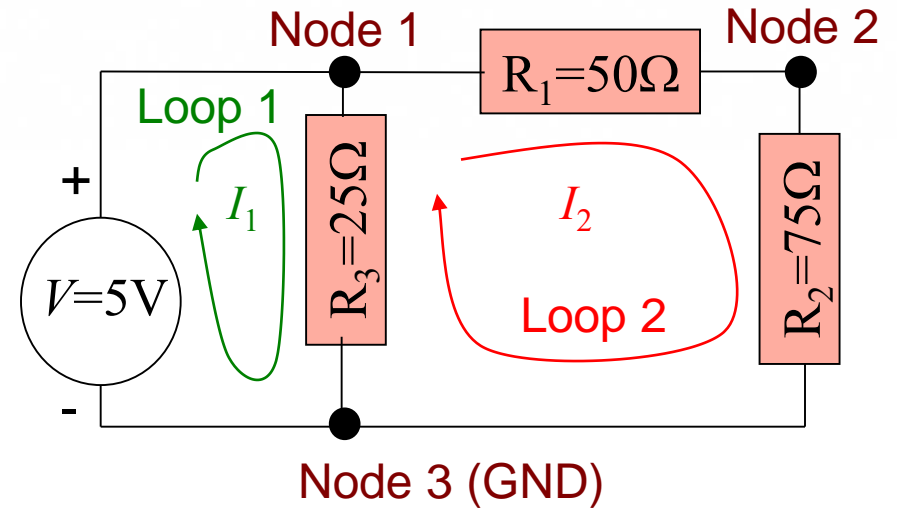
$$\Rightarrow \begin{cases} I_1 = 0.24A \\ I_2 = 0.04A \end{cases}$$



❖ Solutions:

$$V_1 = 5 \text{ V}$$

$$V_2 = I_2 R_2 = 0.04 \times 75 = 3 \text{ V}$$

$$I_{R1} = I_{R2} = I_2 = 0.04 \text{ A}$$

$$I_{R3} = I_1 - I_2 = 0.2 \text{ A}$$

$$I_V = I_1 = 0.24 \text{ A}$$




KCL EXAMPLE

- ❖ Step 1: count the nodes and define all current directions (one node can be designated as 0 or ground and ignored)
- ❖ Step 2: write the node equations
- ❖ Step 3: express branch current using node voltages

$$\text{N1: } I_V + I_{R3} + I_{R1} = 0$$

$$\text{N2: } -I_{R1} + I_{R2} = 0$$
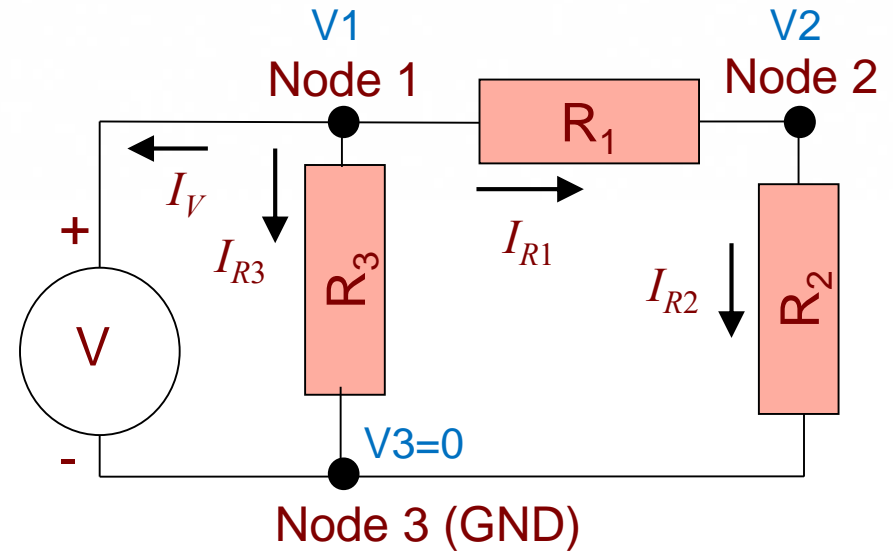
$$\begin{cases} I_V + \frac{V_1}{R_3} + \frac{V_1 - V_2}{R_1} = 0 \\ -\frac{V_1 - V_2}{R_1} + \frac{V_2}{R_2} = 0 \end{cases}$$



- ❖ Step 4: use the known voltage source voltages to eliminate some node voltages

$$\begin{cases} I_V + \frac{V}{R_3} + \frac{V - V_2}{R_1} = 0 \\ -\frac{V - V_2}{R_1} + \frac{V_2}{R_2} = 0 \end{cases} \Rightarrow \begin{cases} I_V - \frac{V_2}{R_1} = -\left(\frac{1}{R_1} + \frac{1}{R_3}\right)V \\ \left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_2 = \frac{V}{R_1} \end{cases}$$






KCL: NUMERICAL EXAMPLE

❖ KCL

$$\begin{cases} I_V - \frac{V_2}{R_1} = -\left(\frac{1}{R_1} + \frac{1}{R_3}\right)V \\ \left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_2 = \frac{V}{R_1} \end{cases}$$

$$\Rightarrow \begin{cases} I_V - \frac{1}{50}V_2 = -\left(\frac{1}{50} + \frac{1}{25}\right)5 \\ \left(\frac{1}{50} + \frac{1}{75}\right)V_2 = \frac{5}{50} \end{cases} \Rightarrow \begin{cases} I_V - \frac{1}{50}V_2 = -\frac{3}{10} \\ \frac{1}{3}V_2 = 1 \end{cases}$$
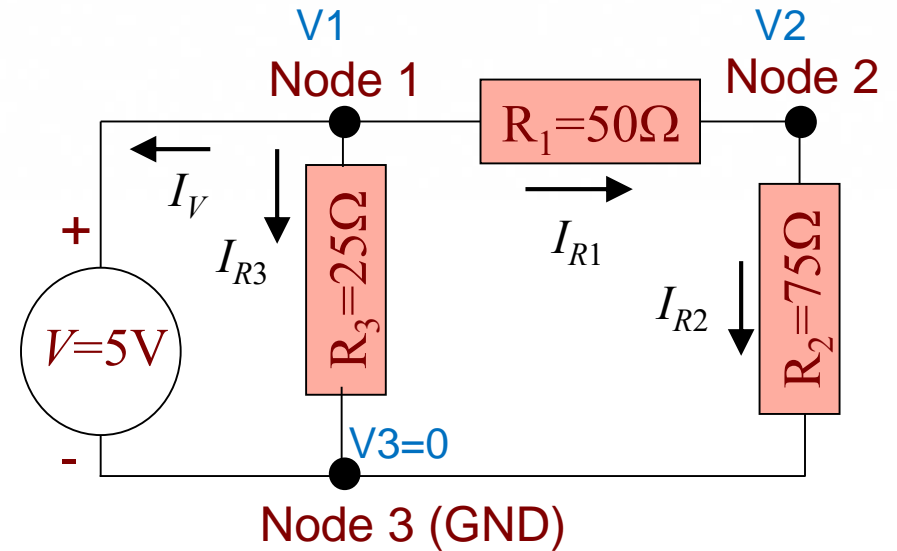
$$\Rightarrow \begin{cases} I_V = -0.24 \text{ A} \\ V_2 = 3 \end{cases}$$



❖ Solutions:

$$V_1 = 5 \text{ V}$$

$$I_{R1} = (V_1 - V_2)/R_1 = 0.04 \text{ A}$$

$$V_2 = 3 \text{ V}$$

$$I_{R2} = V_2/R_2 = 0.04 \text{ A}$$

$$I_V = -0.24 \text{ A}$$


$$I_{R3} = V_1/R_3 = 0.2 \text{ A}$$





CIRCUIT SIMPLIFICATION

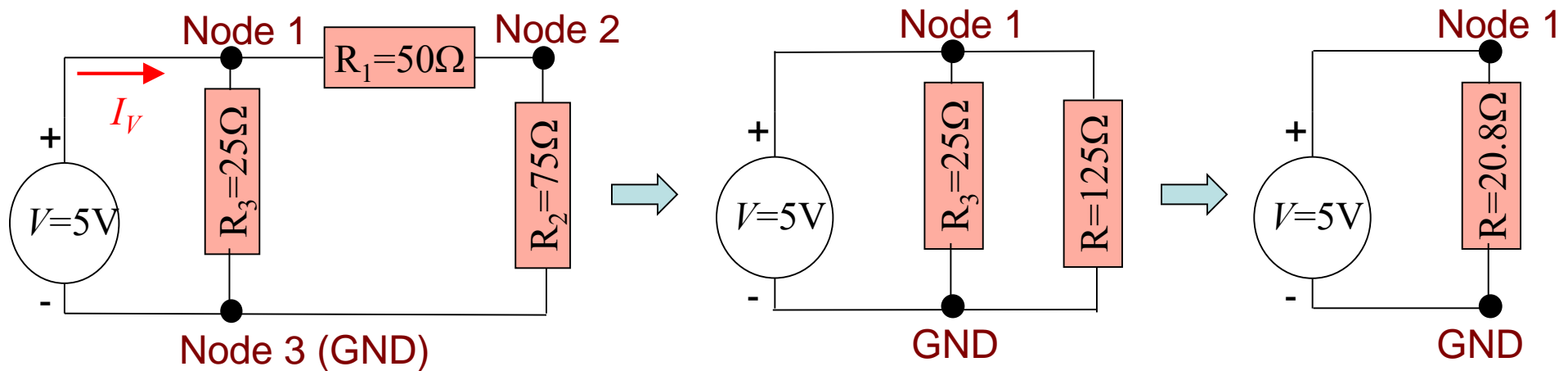- ❖ In the given circuit, we can simplify the circuit and solve individual value **without using KVL or KCL**
- ❖ Example: to find I_V




- ❖ Then apply Ohm's law to find the current




SIMPLIFICATION PROCEDURE

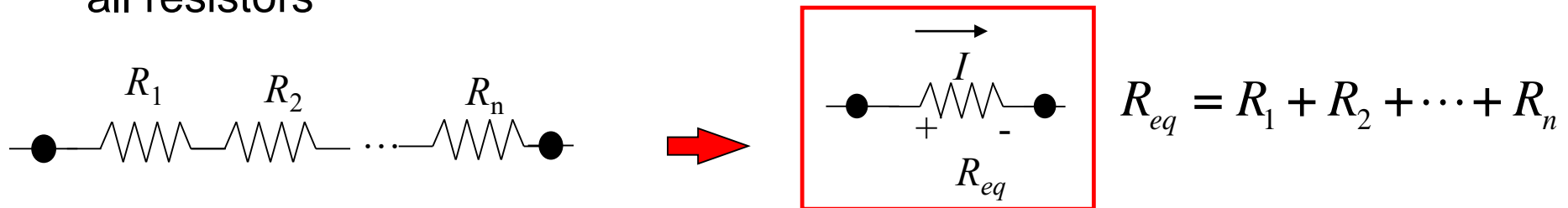- ❖ All branch voltage in parallel with one voltage source is known
- ❖ All branch current in series with one current source is known
- ❖ For resistors in series, replace it with a resistor equal to the sum of all resistors



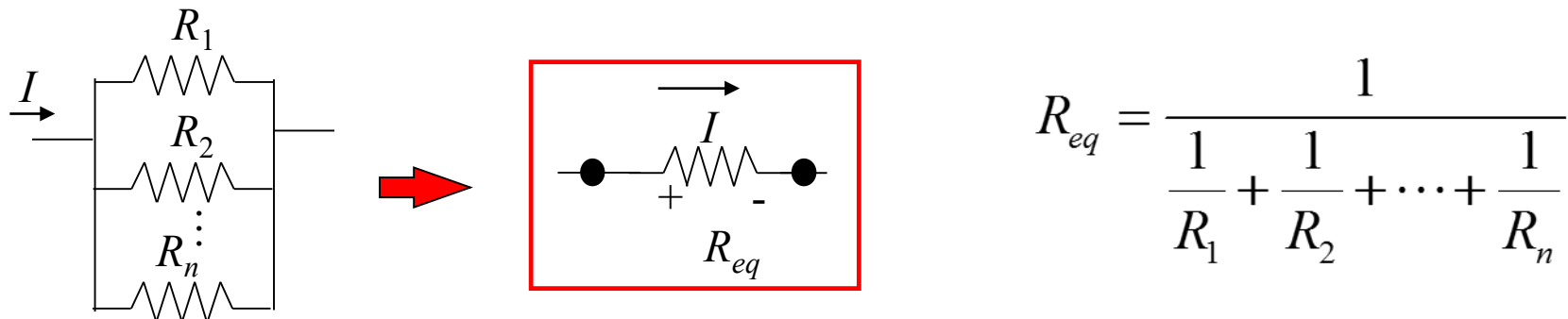
- ❖ Resistors in parallel can also be combined by





ANOTHER CIRCUIT EXAMPLE

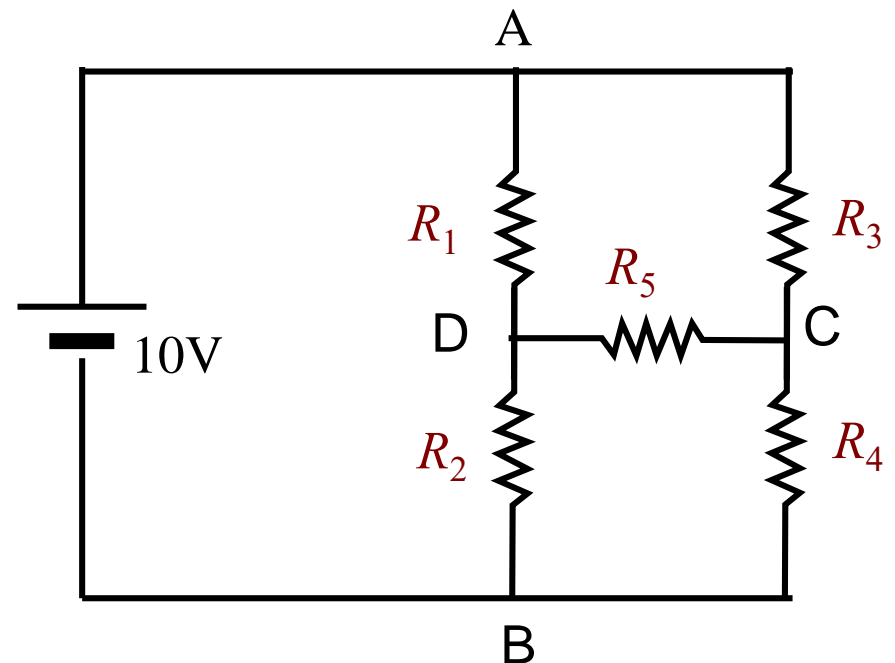- ❖ Consider the given circuit, can you determine the total current from the 10V source by simplifying the circuit?
- ❖ How many **nodes** are there?
- ❖ How many **branches** in the circuit?






DEFINING LOOPS

❖ Step 1: Defining all loops

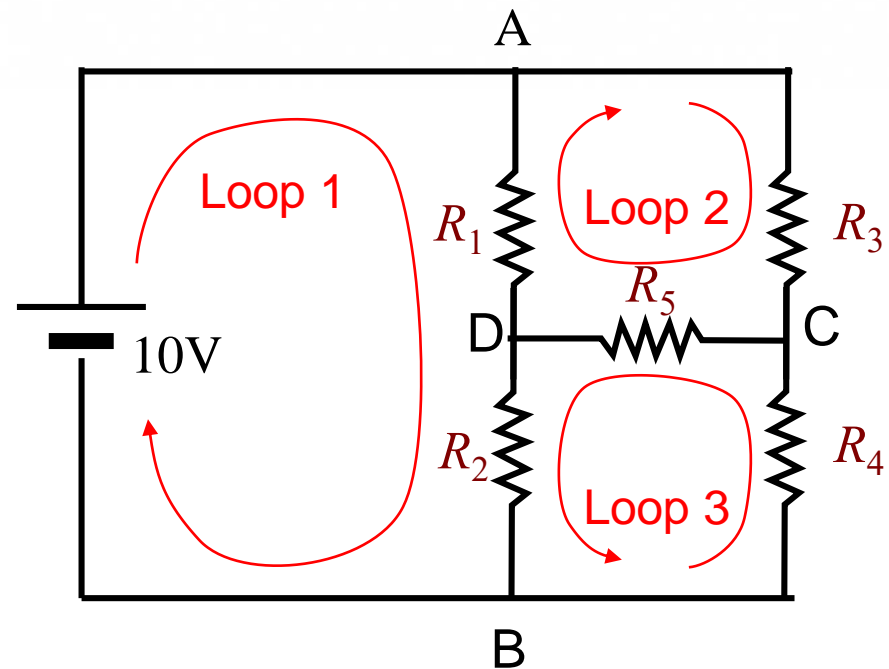- ❖ Is there any branch not covered by the loops?
- ❖ Any other ways you want to define the loops?





WRITING LOOP EQUATIONS

❖ Step 2: Writing the loop equations

➤ Loop 1


$$V_{AD} + V_{DB} - 10 = 0$$

➤ Loop 2

$$V_{AC} + V_{CD} + V_{DA} = 0$$

➤ Loop 3

$$V_{BC} + V_{CD} + V_{DB} = 0$$

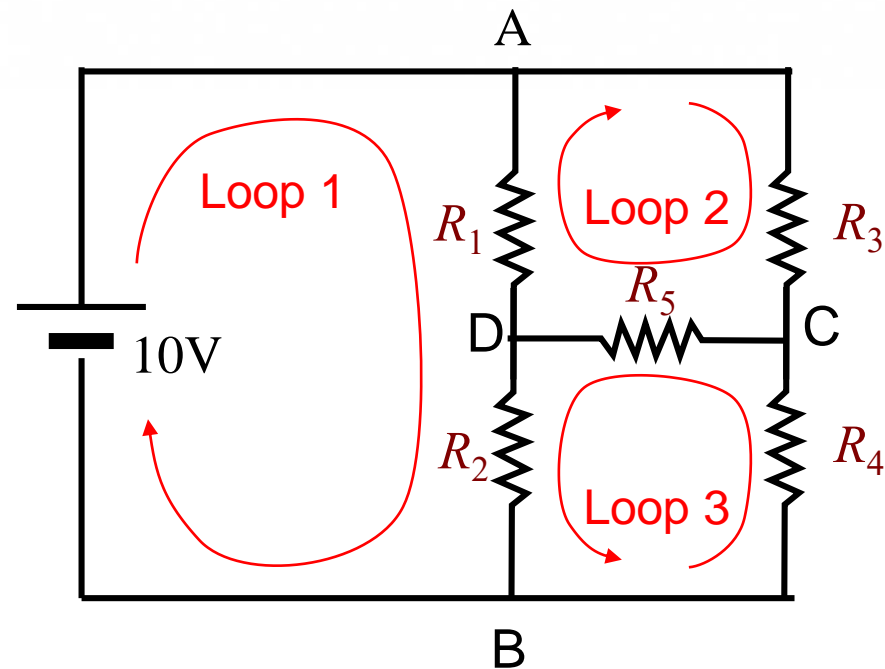



CONVERTING TO LOOP CURRENTS

❖ Step 3: Express in terms of loop currents

➤ Loop 1

$$V_{AD} + V_{DB} - 10 = 0$$

$$\Rightarrow (I_1 - I_2)R_1 + (I_1 + I_3)R_2 = 10$$

➤ Loop 2


$$V_{AC} + V_{CD} + V_{DA} = 0$$

$$\Rightarrow I_2R_3 + (I_2 + I_3)R_5 + (I_2 - I_1)R_1 = 0$$

➤ Loop 3

$$V_{BC} + V_{CD} + V_{DB} = 0$$
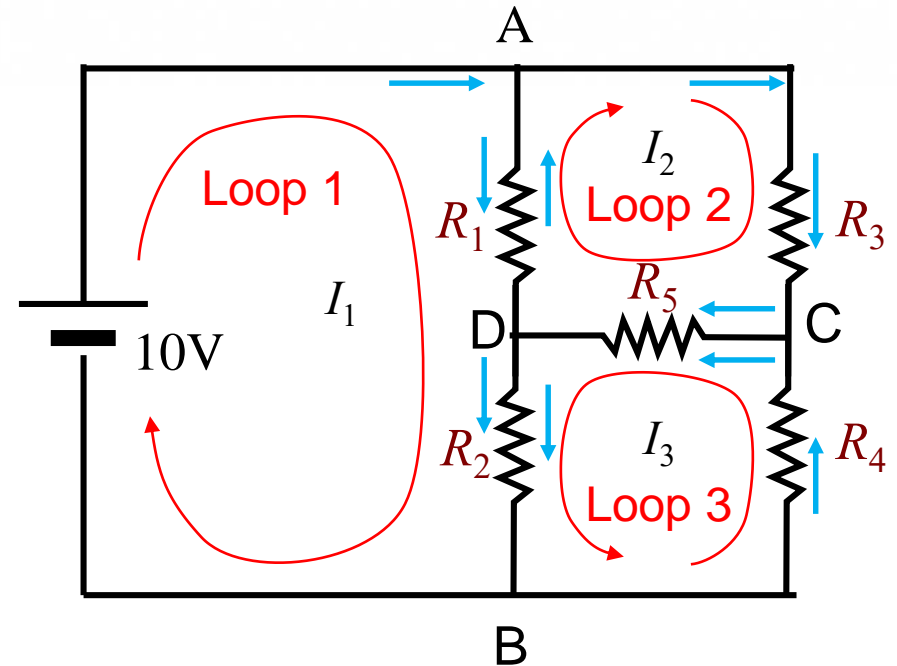
$$\Rightarrow I_3R_4 + (I_2 + I_3)R_5 + (I_1 + I_3)R_2 = 0$$





SOLVING THE SYSTEM OF EQUATIONS

❖ Rewrite the equations

$$(R_1 + R_2)I_1 - R_1I_2 + R_2I_3 = 10$$

$$-R_1I_1 + (R_1 + R_3 + R_5)I_2 + R_5I_3 = 0$$

$$R_2I_1 + R_5I_2 + (R_2 + R_4 + R_5)I_3 = 0$$

❖ Solve for I_1 , I_2 and I_3

❖ Calculate branch currents and node voltages


$$I_{R1} = I_1 - I_2$$

$$I_{R3} = I_2$$

$$I_{R5} = I_2 + I_3$$

$$I_{R2} = I_1 + I_3$$

$$I_{R4} = I_3$$

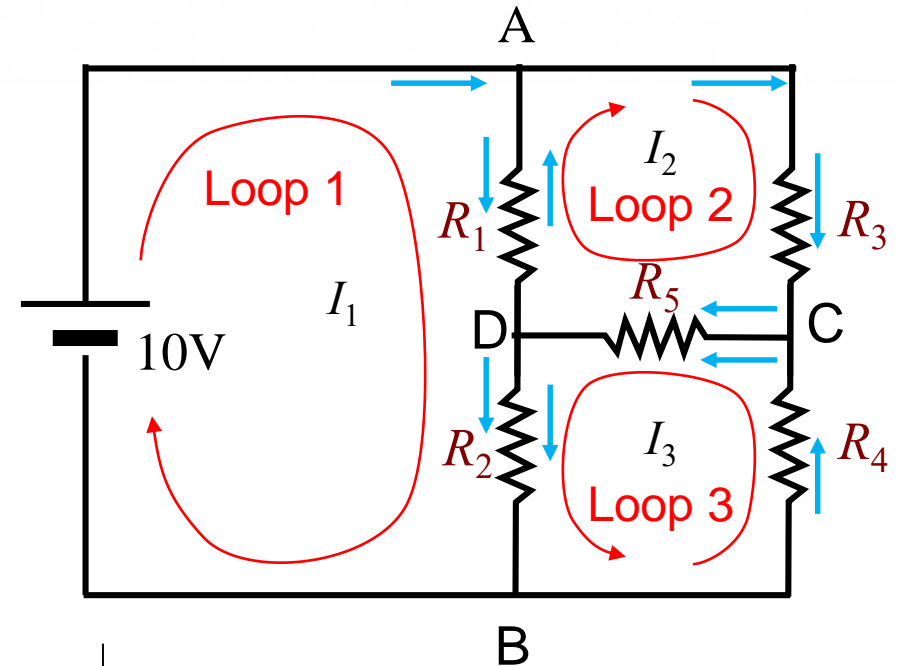

$$V_{AB} = 10V$$

$$V_{DB} = I_{R2}R_2$$

$$V_{CB} = -I_{R4}R_4$$





SOLVING FOR VOLTAGE


- ❖ The resistor values are given by:

$$R_1=100\Omega, R_2=200\Omega, R_3=300\Omega,$$

$$R_4=400\Omega \text{ and } R_5=500\Omega$$

- ❖ Solve for I_1 , I_2 and I_3 ; we have the approximate solution of
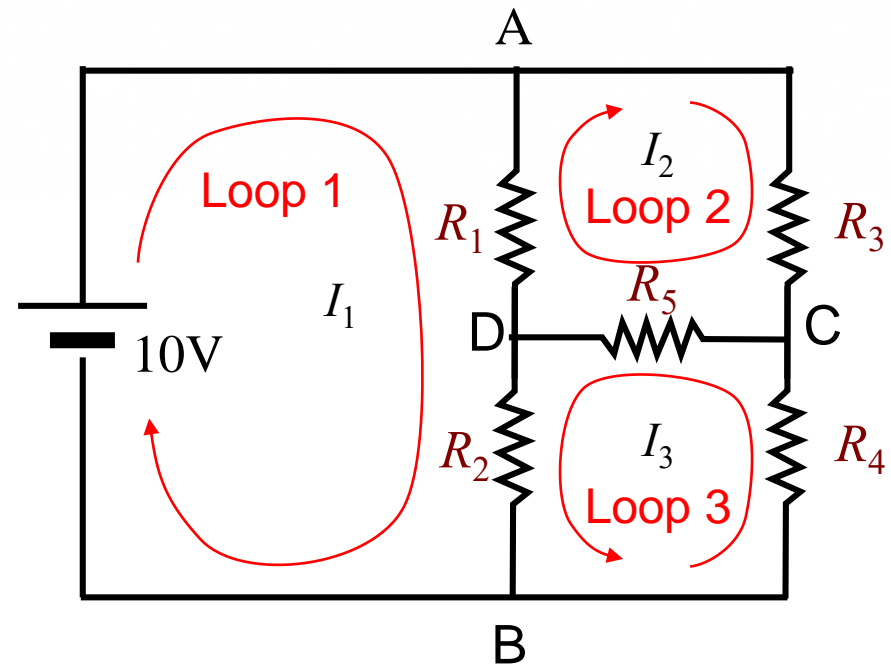
$$I_1 = 48\text{mA}; \quad I_2 = 14\text{mA}; \quad I_3 = -15\text{mA};$$





CAD TOOLS

- ❖ If the network has many components, the number of variables and equations too large to solve by hand calculation
- ❖ Have to rely on computer software program to solve these complex systems
- ❖ We call this a computer-aided design (CAD) tool
- ❖ You will learn how to use CAD tools in other design courses





LECTURE SUMMARY


❖ Kirchhoff's Current Law

- the algebraic sum of all branch currents entering and leaving a node is zero at all instants of time

❖ Kirchhoff's Voltage Law

- the algebraic sum of all branch voltages around any close loop of a network is zero at all instants of time

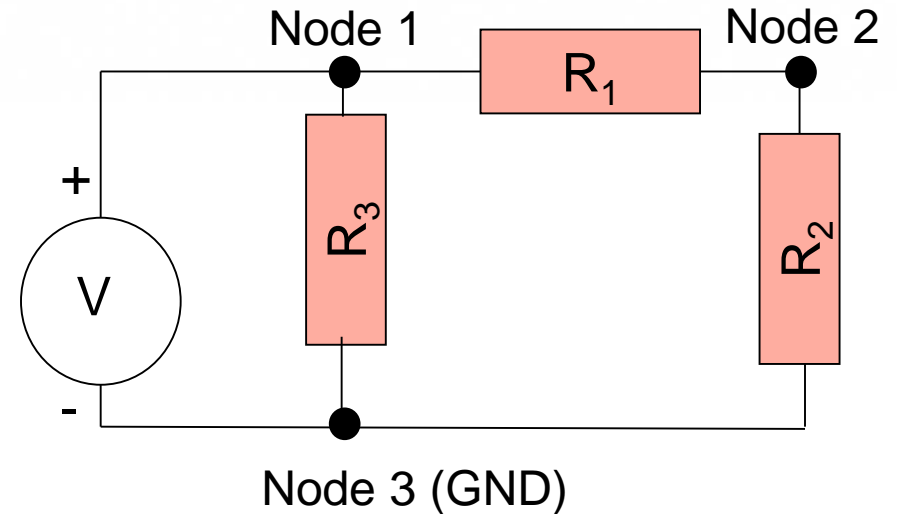- ❖ We have demonstrated how to use KVL and KCL to solve a simple circuit together





NEXT LECTURE

- ❖ Sensors
- ❖ Amplification of sensor signals
- ❖ Lab Midterm Review



QUESTIONS?

